

EE 11L: Circuits Laboratory I

Experiment #2 Simple Resistive Networks

Name: Lawrence Liu
UID: 405749034
Due Date: Nov. 11, 2100

Objectives

To understand how to apply Thevenin and Norton equivalence theorems. To experimentally verify and measure the principle of superposition. To understand the operation of the Wheatstone bridge, and to apply to constructing circuits with sensors.

Theory

Superposition: For a linear circuit, the voltage at any node or current at any branch can be the algebraic sum of the caused by each source acting alone.

Norton and Thevenin Equivalent Circuits: A source Circuit can be converted to its Norton and Thevenin Equivalent Circuits.

The Thevenin equivalent circuit would consist of a voltage source V_{th} in series with a resistor R_{th} . V_{th} is just the voltage across the terminals when open circuited. R_{th} can be found by setting all the independent sources to 0, ie replacing all voltage sources with shorts and replacing all current sources with an open circuit.

The Norton equivalent circuit consists of a current source I_{no} in parallel with a resistor R_{no} . $R_{no} = R_{th}$ and we can find I_{no} by shorting the terminals and measuring the resistance that flows across.

Experiment Setup: Lab 1

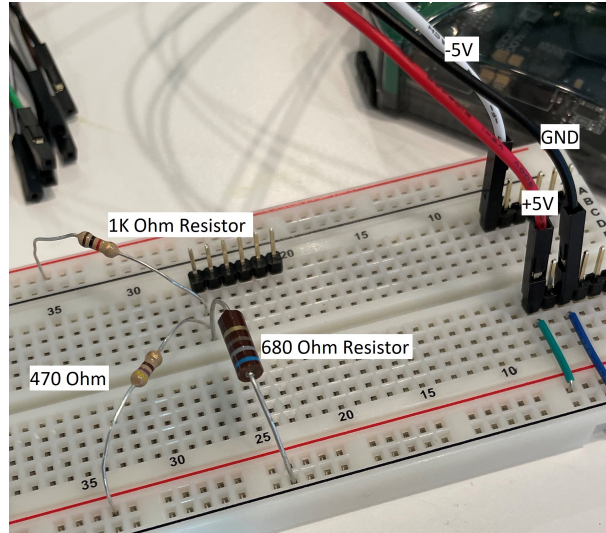


Figure 1: Lab 1 Setup

Measurements: Lab 1

Sources	Voltage (V)	Current (A)
+5V only	2.38V	3.5mA
-5V only	-1.153V	-1.7mA
Sum	1.227V	1.804mA
Both on	1.253V	1.8mA

The theoretical calculations for the voltage across R_3 from the +5V source only is 2.3135V. The theoretical calculations for the voltage across R_3 from the -5V source only is -1.087V. The theoretical calculations for the voltage across R_3 from both sources is 1.226V.

Discussion: Lab 1

The difference between the theoretical and measured voltage for the voltage across R_3 from the +5V source is 2.8%. The difference between the theoretical and measured voltage for the voltage across R_3 from the -5V source is 5.69%. The difference between the theoretical and measured voltage for the voltage across R_3 with both sources on is 2.1%.

Experiment Setup: Lab 2

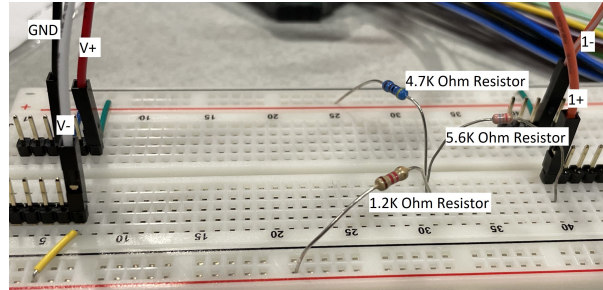


Figure 2: Lab 2 Open Source Circuit

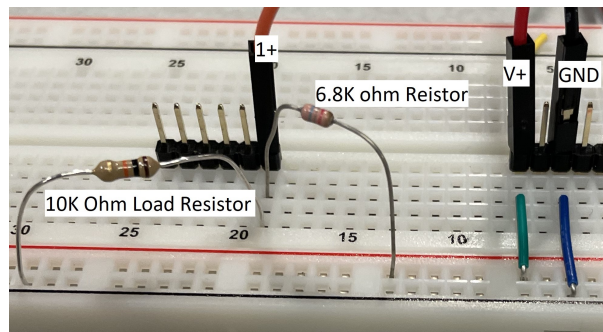


Figure 3: Lab 2 Equivalent Circuit

Measurements: Lab 2

V_{th}	I_N	R_{th}	V_{OC}	I_{SC}	R_{eq}
2.966V	0.452mA	$6.56K\Omega$	2.97V	0.432mA	$6.827K\Omega$

The equivalent circuit I created was a 6.8Ω resistor in parallel with a $2.97V$ voltage source. The voltage across the load resistor in this case was $1.777V$ compared with $1.79V$ in the actual circuit.

Discussion: Lab 2

For the comparison of the voltages across the load resistors in the actual and equivalent circuit, see the measured voltages above.

The power dissipated by the load resistor is

$$P_{R_L} = \frac{R_L}{(R_{th} + R_L)^2} V_{th}^2$$

This is maximized when $R_L = R_{th}$.

Experiment: Lab 3

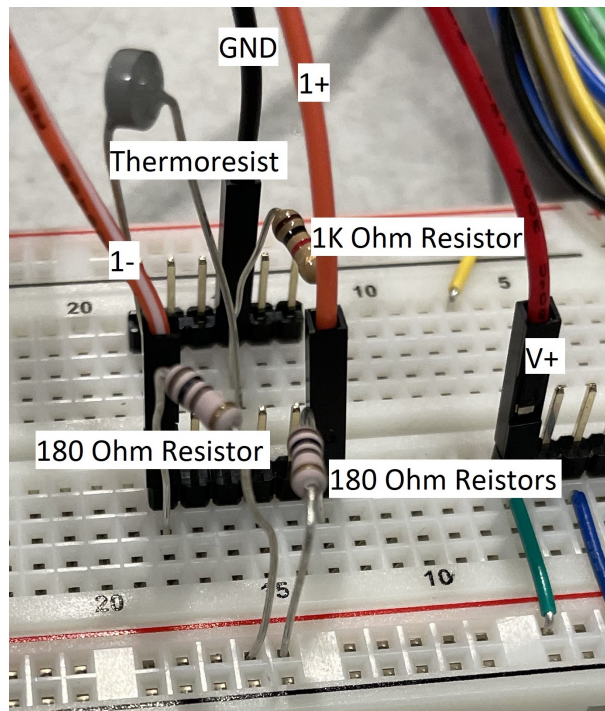


Figure 4: Lab 2 Equivalent Circuit